

Organization of Digital Computer Lab  
EECS112L/CSE 132L

**Assignment 3**  
**Single-cycle MIPS - Complete**

prepared by: Team Stressed

Student name:

Mansi Tyagi

Student ID:

23334840

Student name:

Erik Henriquez

Student ID:

57374677

Student name:

Kevin Chau

Student ID:

76934313

Student name:

Steven Chow

Student ID:

70916812

Student name:

Paul Dao

Student ID:

30658761

EECS Department  
Henry Samueli School of Engineering  
University of California, Irvine

February 21, 2016

# 1 Summary of Processor Design

## 1.1 What We Learned

After implementing a subset of MIPS R-type and I-type instructions in Lab 2, we implemented additional I-type instructions and added support for J-type instructions. After reviewing material we had previously learned in CSE 132, we were able to implement a complete single-cycle processor that met this assignment's specifications. For the synthesis portion of this assignment, we learned to use Synopsys for elaboration and to determine the power consumption, area requirements, and clock frequency necessary to build our processor design. Although the use of Synopsys was initially very troublesome, we appreciated the fact that we were able to use tools that well-known corporations, like Intel and AMD, use to design and fabricate their own products.

## 1.2 Description

For our complete single-cycle processor, we designed ten components: a Program Counter (PC), Controller, Instruction Memory (two versions), Register File, Arithmetic Logic Unit (including a Comparator), Data Memory (RAM), Adders, and the Processor entity. While most of these components existed in our previous processor design, they were all improved and/or modified to work with our new datapath design. The PC no longer increments an initialized variable every clock cycle; instead, it takes in an inputted address and outputs it every clock cycle, basically acting as a register. Our controller has a Branch port (that is being used) and a new Jump port, to enable the use of Branch and J-type instructions, respectively. During simulation, we use the same instruction memory (ROM) component, but we also wrote a ROM for synthesis that has instructions preloaded into its memory array. We changed the design of our Register File so it no longer used WAIT statements, which cannot be synthesized. Our ALU is roughly the same as before, with the exception of the missing Jump port that was moved to the Controller. Our Data Memory was also modified for synthesis, although we chose to use Professor Yaghini's SRAM component for our synthesis results. We created an Adder component to use for our Branch/Jump datapath. Finally, we updated the design of the Processor entity to include all our components and used combinational logic to mimic the multiplexors and logic gates needed along the datapath.

The processor now supports the following branch and J-type instructions: beq, bne, bltz, bgez, blez, bgtz, jump, jr, jal and jalr. To support these instructions, we created a separate Branch/Jump datapath. Composed of two Adder components and combinational logic that acts as the required Shifters and Multiplexors, the new datapath runs alongside our old one. For branch instructions, the Controller and ALU must send branch signals before the PC can be changed appropriately. To do this, the Controller must recognize the instruction as a Branch instruction from the OpCode and the ALU must check if the branch condition (register equivalency, register difference, etc.) is met. For J-type instructions, only the Controller's Jump signal is needed to allow the modification to the PC.


## 1.3 Testbench Architecture

For the most part, our testbench is the same as the one that we used for our Lab 2 assignment. We added more cycles to accommodate for the additional instructions in our Instruction Memory. For example, we run two beq instructions (one fails and the other succeeds) and a jump instruction that goes into uninitialized memory.

# 2 Sample Program

## 2.1 Simulation Waveform

Simulation Waveform is as follows:

 

### 3.3 Required Frequency

According to the generated timing report, our Critical Path Length was 3.16 ns. In order to accommodate this and eliminate negative slack, we raised our clock period from 2.0 ns to 3.18 ns. This results in a frequency of approximately 314.5 MHz.

## 4 Known Issues

For the instructions used for Questasim to simulate the processor that we designed, we used the same example instructions as last time for the testbench where we read line by line, one instruction at a time, from a file. For synthesis, we created a second version of instruction memory that has instructions preloaded into memory in order to synthesize the Processor properly.

## 5 Conclusion

As a complete single-cycle processor, our project now supports a larger subset of the full MIPS instruction set. It is capable of all three types of MIPS instructions: R-type, I-type, and J-type. Through synthesis, we were able to determine the area, power and frequency properties our processor design would have if fabricated. Finally, with this complete processor, we should be well prepared to implement pipelining in our future assignment.